

UNIVERSITY OF SWAZILAND
FACULTY OF SCIENCE
Department of Electronic and Electrical Engineering

MAIN EXAMINATION 2015

Title of the Paper:

Analogue Design I

Course Code: **EE321**

Time Allowed: **Three Hours.**

Instructions:

1. To answer, pick any to sum a total of 100% from 8 questions in the following pages.
2. The answer must be written in the space provided in the question book. Use the answer book as a scratch pad.
3. This paper has 11 pages, including this page.

**DO NOT OPEN THE PAPER
UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.**

Q1: (20 pts) Give low and high frequency equivalent circuits respectively of BJT and FET. All component values must be marked correctly according to the given data from the data-sheet and each circuit must have its title. So all together, there are 4 circuits. (5pts each ckt).


Q2: (10 pts) From the given input and output characteristics respectively of BJT (2N3904) and FET (2N3819), find the BJT and the FET low frequency equivalent circuit parameters. (5 pts for each)

Q3: (20 pts) List R_{in} , R_{ot} , A_i , and A_v of the single BJT amplifier of all three configurations, CE, CB, and CC. Pick any 5 to answer.


	R_{in}	R_{ot}
CE		
CB		
CC		

	A_v	A_i
CE		
CB		
CC		

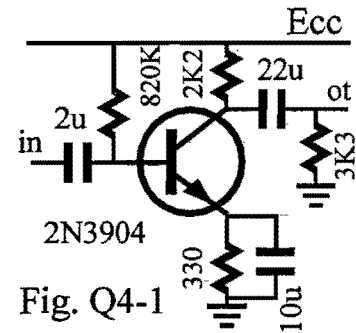
Q4: (20 pts) Use SCTC method, estimate ω_L , for the CE amplifier shown in Fig. Q4-1. The BJT parameters is given in the attached data-sheet. (5 pts for each time constant and 5 pts for the final result)



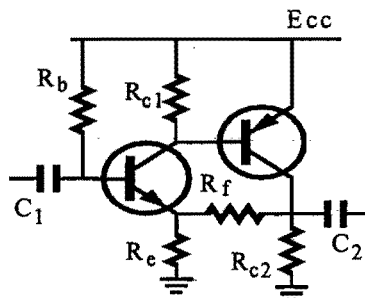Q5: (20 pts) A 2-BJT linear feedback amplifier is shown on the right. (5 pts) Identify whether the feedback is positive or negative and its feedback topology (s-s, s-p, p-s, p-p). Find (i). (5 pts) A_o and (5 pts) A_f and (ii). (5 pts) β and check if $\beta = R_e / (R_e + R_f)$. For numerical calculation, the component values are given as the following: Signal source: $R_s = 0$; Circuit components in Ohms: $R_{C1} = 8K$, $R_{C2} = 2K$, $R_e = 0.2K$, $R_f = 8K$ and BJT parameters $h_{ie} = 2K$, $h_{fe} = 120$. Consider the two BJT has the same parameters. (hint: First, set R_f symbolical and all the rest numerical and calculate voltage gain. Secondly, calculate open loop gain A_o as $R_f \rightarrow \infty$. Calculate A_f as $R_f = 8K$) (10 pts each)



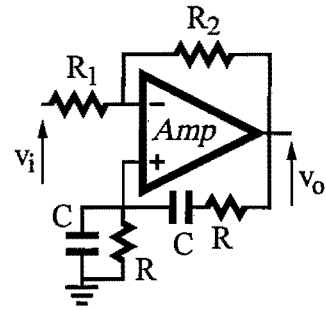Q6: (10 pts) A Wien amplifier is shown on the right. (i). Derive the voltage amplification factor in terms of the component symbols, given $R_s=0$. (ii). Discuss the stability of the amplifier in terms of the resistor ratio, $R_2/R_1=\eta$; that is, discuss the boundary of η . On one side of the boundary, the circuit is a stable BPF amplifier; while on the other side the circuit is a frequency oscillator. (5 pts each)



Q7: (10 pts) 2N3055 has a power dissipation rating 115 Watts at case temperature 25°C , a maximum junction temperature 200°C , and thermal resistance from junction to case $\theta_{jc}=1.25\text{ C/W}$. To maintain a case temperature 25°C needs an infinitively large heat sink, which is not possible. (i) Study the relationship between the power dissipation rating, P_D , and case temperature, T_C . Draw the curve $P_D \sim T_C$. (ii) Design a practical heat sink to dissipate the heat to the air at a temperature 25°C . Assume the transistor case and heat sink have a perfect thermal contact. Case temp may be around 45°C ; calculate sink θ_{ca} , where ca is between the case and the air. Find the new power dissipation again, (5 pts for curve, 5 pts for sink θ_{ca} and new P_D)

Q8: (20 pts) An amplifier has a voltage amplification factor:

$$A(s) = \frac{2\pi \cdot 10^9 \cdot s}{(s + 2\pi \cdot 10^3)(s + 2\pi \cdot 10^5)}$$

- (i). Draw the frequency response in Bode form; find mid-band gain; and find the dominant ω_L and ω_H . (ii). If use feedback technique and reduce the mid-band gain to 200, what are the new dominant ω_L and ω_H . (10 pts for each)

UMT3904 / SST3904 / MMST3904 / 2N3904

Transistors

NPN General Purpose Transistor

UMT3904 / SST3904 / MMST3904 / 2N3904

●Electrical characteristics (Ta = 25°C)

Parameter	Symbol	Min.	Typ.	Max.	Unit	Conditions
Collector-base breakdown voltage	BV _{CEO}	60	-	-	V	I _c = 10μA
Collector-emitter breakdown voltage	BV _{CE0}	40	-	-	V	I _c = 1mA
Emitter-base breakdown voltage	BV _{EB0}	6	-	-	V	I _e = 10μA
Collector cutoff current	I _{CEs}	-	-	50	nA	V _{CE} = 30V
Emitter cutoff current	I _{EB0}	-	-	50	nA	V _{EB} = 3V
Collector-emitter saturation voltage	V _{CE(sat)}	-	-	0.2	V	I _c /I _b = 10mA/1mA
		-	-	0.3		I _c /I _b = 50mA/5mA
Base-emitter saturation voltage	V _{BE(sat)}	0.65	-	0.85	V	I _c /I _b = 10mA/1mA
		-	-	0.95		I _c /I _b = 50mA/5mA
DC current transfer ratio	h _{FE}	40	-	-	-	V _{CE} = 1V, I _c = 0.1mA
		70	-	-		V _{CE} = 1V, I _c = 1mA
		100	-	300		V _{CE} = 1V, I _c = 10mA
		60	-	-		V _{CE} = 1V, I _c = 50mA
		30	-	-		V _{CE} = 1V, I _c = 100mA
Transition frequency	f _r	300	-	-	MHz	V _{CE} = 20V, I _e = -10mA, f = 100MHz
Collector output capacitance	C _{ob}	-	-	4	pF	V _{CB} = 10V, f = 100kHz
Emitter input capacitance	C _{ib}	-	-	8	pF	V _{EB} = 0.5V, f = 100kHz
Delay time	t _d	-	-	35	ns	V _{CC} = 3V, V _{BE(OFF)} = 0.5V, I _c = 10mA, I _{B1} = 1mA
Rise time	t _r	-	-	35	ns	V _{CC} = 3V, V _{BE(OFF)} = 0.5V, I _c = 10mA, I _{B1} = 1mA
Storage time	t _{stg}	-	-	200	ns	V _{CC} = 3V, I _c = 10mA, I _{B1} = -I _{B2} = 1mA
Fall time	t _f	-	-	50	ns	V _{CC} = 3V, I _c = 10mA, I _{B1} = -I _{B2} = 1mA

●Electrical characteristic curves

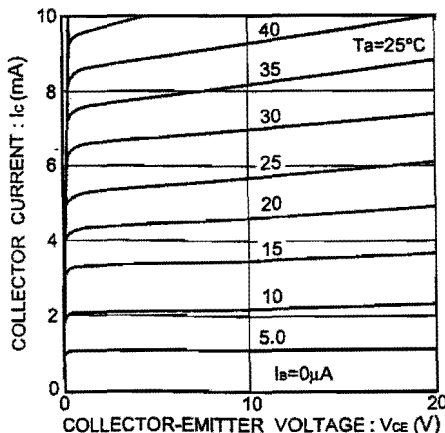


Fig.1 Grounded emitter output characteristics

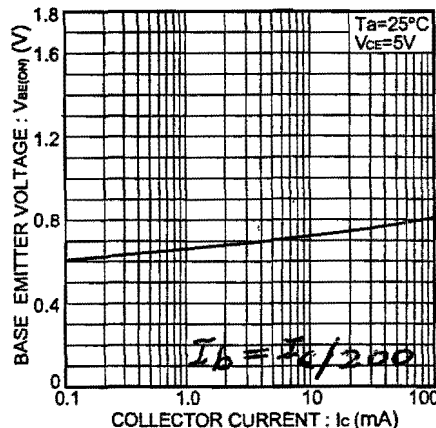


Fig.7 Grounded emitter propagation characteristics

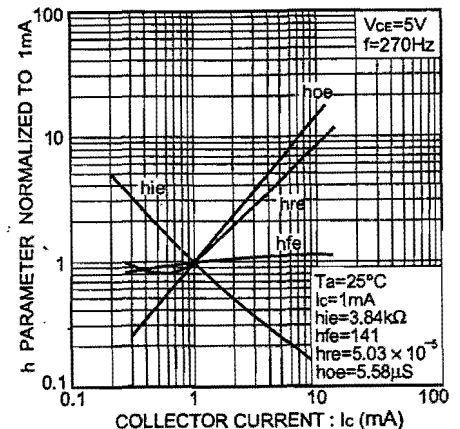


Fig.15 h parameter vs. collector current



SPECIFICATIONS (T_A = 25°C UNLESS OTHERWISE NOTED)

Parameter	Symbol	Test Conditions	Limits			Unit	
			Min	Typ ^a	Max		
Static							
Gate-Source Breakdown Voltage	V _{(BR)GSS}	I _G = -1 μA, V _{DS} = 0 V	-25	-35		V	
Gate-Source Cutoff Voltage	V _{GS(off)}	V _{DS} = 15 V, I _D = 2 nA		-3	-8		
Saturation Drain Current ^b	I _{DSS}	V _{DS} = 15 V, V _{GS} = 0 V	2	10	20	mA	
Gate Reverse Current	I _{GSS}	V _{GS} = -15 V, V _{DS} = 0 V T _A = 100°C		-0.002	-2	nA	
				-0.002	-2	μA	
Gate Operating Current ^c	I _G	V _{DG} = 10 V, I _D = 1 mA		-20		pA	
Drain Cutoff Current	I _{D(off)}	V _{DS} = 10 V, V _{GS} = -8 V		2		pA	
Drain-Source On-Resistance	r _{DS(on)}	V _{GS} = 0 V, I _D = 1 mA		150		Ω	
Gate-Source Voltage	V _{GS}	V _{DS} = 15 V, I _D = 200 μA	-0.5	-2.5	-7.5	V	
Gate-Source Forward Voltage	V _{GS(F)}	I _G = 1 mA, V _{DS} = 0 V		0.7			
Dynamic							
Common-Source Forward Transconductance ^c	g _{fs}	V _{DS} = 15 V V _{GS} = 0 V	f = 1 kHz	2	5.5	6.5	mS
			f = 100 MHz	1.6	5.5		
			f = 1 kHz		25	50	
Common-Source Output Conductance ^c	g _{os}	V _{DS} = 15 V, V _{GS} = 0 V, f = 1 MHz		2.2	8	pF	
Common-Source Input Capacitance	C _{iss}			0.7	4		
Common-Source Reverse Transfer Capacitance	C _{rss}						
Equivalent Input Noise Voltage ^c	e _n	V _{DS} = 10 V, V _{GS} = 0 V, f = 100 Hz		6		nV/ √Hz	

Notes

- a. Typical values are for DESIGN AID ONLY, not guaranteed nor subject to production testing.
- b. Pulse test: PW ≤ 300 μs, duty cycle ≤ 2%.
- c. This parameter not registered with JEDEC.

NH

TYPICAL CHARACTERISTICS (T_A = 25°C UNLESS OTHERWISE NOTED)

