

**UNIVERSITY OF SWAZILAND**

**FACULTY OF SCIENCE**

**DEPARTMENT OF PHYSICS**

**MAIN EXAMINATION 2005**

**TITLE OF PAPER : ELECTRONICS (PAPER 1)**

**COURSE NUMBER : P310 (i)**

**TIME ALLOWED : THREE HOURS**

**INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE  
QUESTIONS**

**EACH QUESTION CARRIES 25 MARKS**

**MARKS FOR DIFFERENT SECTIONS ARE  
SHOWN IN THE RIGHT-HAND MARGIN.**

**THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE.**

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE  
INVIGILATOR.**

### QUESTION 1

- (a) An RLC bandpass filter is to be designed using a 10 mH inductor whose resistance is  $75\ \Omega$ . The centre frequency of the filter is to be 25 kHz.
- (i) What value of capacitance should be used? (4 marks)
  - (ii) If the bandwidth of the filter is to be made less than 2500 Hz, what is the quality factor? (3 marks)
- (b) For the high-pass filter shown in Fig. 1.1:
- (i) Find the cut-off frequency in hertz. (3 marks)
  - (ii) Find the magnitude of  $v_{out}$  when  $v_{in}$  has a frequency of 15 kHz and of 100 kHz. (5 marks)
  - (iii) Find the phase angle between  $v_{out}$  and  $v_{in}$ , when  $v_{in}$  has a frequency of 20 kHz and that of 80 kHz. (5 marks)
- (c) An RC low-pass filter is to be designed to create a  $60^\circ$  phase lag in a 2.5 kHz signal. If the filter capacitance is  $0.2\ \mu\text{F}$ , what value of resistance should be used? (5 marks)

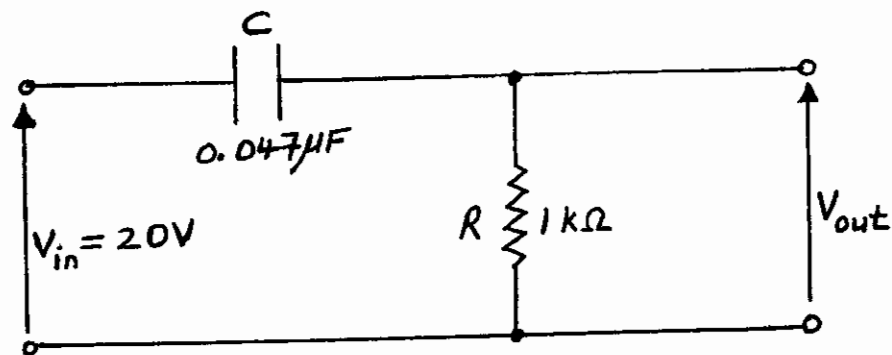


Fig. 1.1

## QUESTION 2

- (a) The drain current in a junction field effect transistor (JFET) amplifier varies by  $\pm 1$  mA when a signal voltage with a peak-to-peak value of 2 V is applied at the input of the amplifier.

Calculate the transconductance,  $g_m$  of the transistor.

(3 marks)

- (b) The I-V characteristics of a **p-channel** JFET may be plotted when the following equipment/components are available for current and voltage measurements:  
d.c. power supplies, potentiometers, a d.c. ammeter and a d.c. voltmeter.

- (i) Draw and label the diagram of a circuit you would use to measure the values of current and voltage. (4 marks)

- (ii) Sketch typical transfer and drain characteristic curves for this type of JFET. Label them.

(5 marks)

- (c) (i) Draw and label a self-biasing common-source amplifier which utilises an n-channel junction field effect transistor. The diagram should include all capacitors and resistors required in the circuit. (3 marks)

- (ii) Draw a small signal equivalent circuit and label it. State the significance of each element shown in the equivalent circuit.

(10 marks)

### QUESTION 3

- (a) With reference to a labelled schematic diagram, discuss the principle of operation of an npn bipolar junction transistor. (9 marks)
- (b) The values of the leakage current  $I_{CEO}$  in a bipolar junction transistor at various junction temperatures are listed below:

Junction temperature ( $^{\circ}\text{C}$ )	20	30	40	50	60
Leakage current, $I_{CEO}$ ( $\mu\text{A}$ )	60	120	240	480	960

This transistor has  $h_{FE} = 100$ . It is used as an amplifier in common-emitter connection with dc bias current of  $30 \mu\text{A}$ .

Calculate the change in collector current,  $I_C$  as the junction temperature rises from  $20^{\circ}\text{C}$  to  $60^{\circ}\text{C}$ . (7 marks)

- (c) With the aid of a small signal model, derive the expression below which represents the voltage gain of an emitter follower.

$$A_V = \frac{(h_{fe} + 1)R_L}{r_{\pi} + (h_{fe} + 1)R_L}$$

(9 marks)

#### QUESTION 4

- (a) Suppose that you were required to build the op-amp circuit shown in Fig. 4.1, which gives a voltage gain of 100. What values of  $R_1$  and  $R_2$  would you need for this purpose? (4 marks)
- (b) Use operational amplifiers to **design** circuits which correspond to each of the following ideal relationships between the output and the input voltage(s):
- (i)  $v_o = -4 \times 10^{-2} \int v_1 dt$  (7 marks)
- (ii)  $v_o = -2 \times 10^{-4} \frac{dv_1}{dt}$  (7 marks)
- (iii)  $v_o = -(3v_1 + 5v_2 + v_3)$  (7 marks)

where  $v_1$ ,  $v_2$  and  $v_3$  are input voltage signals.

(Note: determine suitable values of resistors and capacitors)

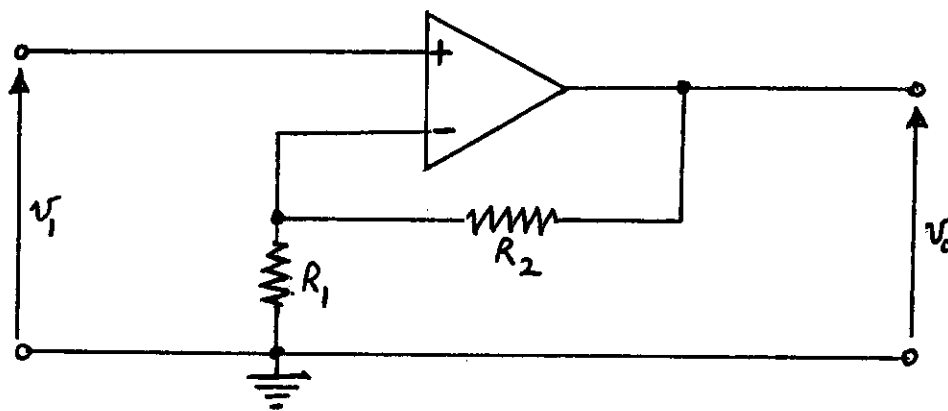


Fig. 4.1

### QUESTION 5

- (a) Calculate the diode current in the circuit shown in Fig. 5.1, assuming that the turn-on voltage is 0.7 V. (4 marks)
- (b) With reference to amplifiers, explain what is meant by degenerative feedback. (3 marks)
- (c) Consider an amplifier with an open-loop gain of -700. Negative feedback is applied to the amplifier and the feedback factor is 0.04.
- (i) What would be the gain with feedback? (3 marks)
- (ii) Calculate the closed-loop gain if the open-loop gain falls by 20%. (5 marks)
- (iii) Calculate the percentage change in closed-loop gain from the results obtained in (i) and (ii). (2 marks)
- (d) (i) Draw the schematic diagram of a phase-shift oscillator and label it. (3 marks)
- (ii) Discuss, briefly, the principle of operation of this oscillator and comment on the attenuation effect of the phase-shift ladder network as well as the Barkhausen criterion. (5 marks)

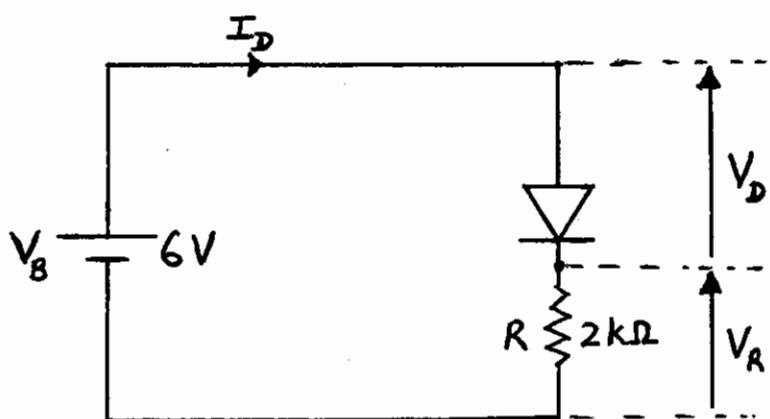


Fig. 5.1