

**UNIVERSITY OF SWAZILAND**

**FACULTY OF SCIENCE AND ENGINEERING**

**DEPARTMENT OF PHYSICS**

**SUPPLEMENTARY EXAMINATION 2016**

**TITLE OF PAPER : ELECTRONICS 1**

**COURSE NUMBER : P311**

**TIME ALLOWED : THREE HOURS**

**INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS**

**EACH QUESTION CARRIES 25 MARKS**

**MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN  
THE RIGHT-HAND MARGIN.**

**THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE.**

**DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE  
INVIGILATOR.**

### QUESTION 1

- (a) The voltage supplied by an a.c. power-line is nominally 120 V r.m.s. The line is connected to a step-down transformer with a turns ratio of 50. Calculate the peak-to-peak secondary voltage of the transformer. (6 marks)
- (b) Fig. 1.1 shows a basic Zener diode voltage regulator. Discuss the principle of operation of this regulator.

State the conditions that should be satisfied to ensure that the regulator gives a constant output voltage and that the diode is not damaged. (11 marks)

- (c) A 9.1 V, 1.3 W Zener diode has a minimum current requirement of 20 mA and is to be used as a voltage regulator. The supply voltage is  $20\text{ V} \pm 10\%$  and the constant load current is 30 mA.
- (i) Calculate the series resistance required; (2 marks)
- (ii) Find the load resistance; (2 marks)
- (iii) How much power is dissipated in the diode when the supply voltage is 22 V? (4 marks)

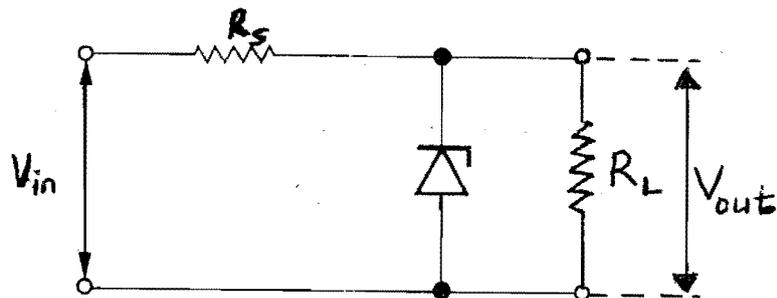


Fig. 1.1

**QUESTION 2**

- (a) Explain what the term ‘hybrid parameters’ means. (3 marks)
- (b) Explain what is wrong with the following statement: “An npn transistor is connected in the common-emitter configuration. The base-emitter junction is forward biased and its collector-base junction is reverse-biased. When the base-emitter voltage is made more negative the collector current is reduced”. (3 marks)
- (c) Consider a bipolar junction transistor amplifier with a collector resistor  $R_C = 2 \text{ k}\Omega$ . The transistor has the following h-parameters:  $h_{fe} = 200$ ,  $h_{ie} = 1 \text{ k}\Omega$  and  $h_{oe} = 2 \times 10^{-5} \Omega^{-1}$ .
- (i) Draw a detailed a.c. equivalent circuit of this amplifier and label it. (3 marks)
- (ii) Find the voltage gain of the amplifier when the output resistance,  $1/h_{oe}$  is neglected ( $1/h_{oe} \gg R_C$ ). (3 marks)
- (d) An npn silicon transistor for which  $h_{FE}$  is 200 is used in a common-emitter amplifier circuit shown in Fig. 2.1, with a potential divider network ( $R_1$  and  $R_2$ ) and emitter resistor  $R_E$  to establish the dc bias conditions. Assuming that  $I_{BB}$ , the current in the potential divider network, is greater than  $10I_B$ , that is  $I_{BB} \gg I_B$ , calculate the values of the direct currents,  $I_E$  and  $I_B$  and the d.c. voltages  $V_B$ ,  $V_C$  and  $V_{CE}$ . Let  $V_{BE} = 0.6 \text{ V}$ . (13 marks)

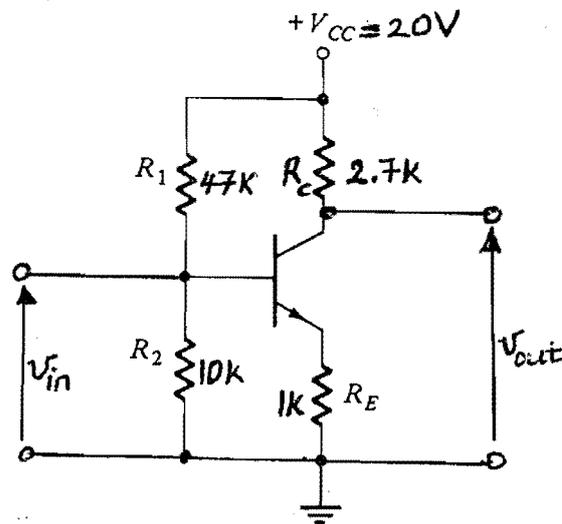


Fig. 2.1

### QUESTION 3

- (a) Explain briefly why a p-n junction diode acts as a rectifier. (3 marks)
- (b) Consider a bridge-rectifier circuit with a filter capacitor  $C$  placed across the load resistor  $R$  for the case in which the transformer secondary delivers a sinusoid of 12 V (rms) having a 60-Hz frequency and assuming  $V_D = 0.7$  V and a load resistance  $R_L = 100 \Omega$ .
- Draw a schematic diagram of the bridge rectifier with a capacitor filter. (2 marks)
  - What is the dc voltage of the output? (4 marks)
  - Find the average current through  $R_L$ . (2 marks)
  - Find the value of  $C$  which results in a peak-to-peak ripple voltage of 1 V. (3 marks)
- (c) The step-down transformer of the full-wave rectifier shown in Fig. 3.1 has a turns ratio of 8:1. The r.m.s. voltage at the secondary of the transformer is 18 V. The load resistance is 1 k $\Omega$  and the diode voltage is 0.6 V. Calculate
- The r.m.s primary voltage. (3 marks)
  - The peak value of the current flowing in the load. (4 marks)
  - The average or d.c. current through the load. (4 marks)

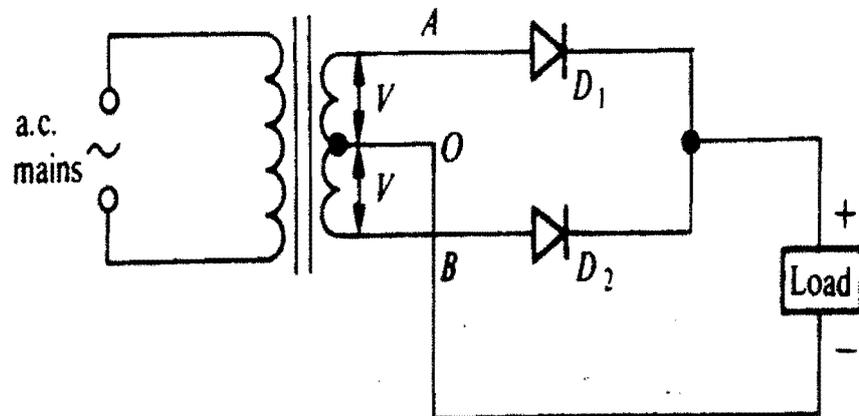


Fig. 3.1

#### **QUESTION 4**

- (a) Use a suitable diagram(s) to explain how you would fabricate a p-channel junction JGFET. (10 marks)
- (b) With the aid of a diagram(s) and characteristics, explain how the transistor referred to in Q. 4(a) above works. (8 marks)
- (c) (i) Draw an a.c. equivalent circuit of an n-channel JFET amplifier connected in the common-source configuration. (3 marks)
- (ii) Show that the voltage gain of the common-source amplifier is given by the following equation:

$$\frac{v_{out}}{v_{in}} = -\frac{g_m}{\frac{1}{R_D} + \frac{1}{r_d}},$$

where the symbols have their usual meanings. (4 marks)

### **QUESTION 5**

- (a) Sketch the energy band diagram of phosphorous-doped n-type silicon and label it. Comment on the meaning of the diagram. (5 marks)
- (b) The Zener diode stabiliser shown on page 2, Fig. 1.1 has an input voltage,  $V_i = 15\text{V}$  and a load resistance,  $R_L = 1.2\text{ k}\Omega$ . The current through the Zener diode is 6 mA and the voltage across the load is 9 V.
- (i) Calculate the value of the series resistance,  $R_S$ . (4 marks)
- (ii) Calculate the diode current when  $R_L = 1\text{ k}\Omega$ . (4 marks)
- (c) (i) Suppose that you were required to measure the characteristics of an n-p-n transistor that is connected in the common-emitter configuration. Draw a diagram to show how you would connect the circuit. Label it. (3 marks)
- (ii) Sketch the output characteristics of the transistor and show the saturation, cut-off and active regions. Label the characteristics. (5 marks)
- (d) Consider an n-channel JUGFET connected in the common-source configuration. Assume that when the gate-source voltage,  $V_{GS}$  is kept constant, a change in the drain-source voltage,  $V_{DS}$  of 1V results in a change in the drain current,  $I_D$  of 0.2 mA.
- Calculate the drain resistance,  $r_d$  of the JUGFET. (4 marks)